

**Question Bank**

**Subject: Digital Techniques (DTE-313303)**

1. Draw logic diagram of T flip-flop and give its truth table.
2. Define modulus of a counter. Write the numbers of flip flops required for Mod-6 counter.
3. Minimize the following expression using K-Map.  
$$f(A, B, C, D) = \sum m (0, 1, 2, 4, 5, 7, 8, 9, 10)$$
4. Describe the function of full Adder Circuit using its truth table, K-Map simplification and logic diagram.
5. Describe the working of JK flip-flop with its truth table and logic diagram.
6. Draw 16:1 MUX tree using 4:1 MUX.
7. Calculate analog output of 4 bit DAC for digital input 1101.  
Assume  $V_{FS} = 5V$ .
8. Design one digit BCD Adder using IC 7483
9. Describe the operation of R-S flip flop using NAND gates only .
10. Give classification of memory
11. State the applications of shift register.
12. Convert the following expression into standard SOP form.  
$$Y = AB + A^{\neg} + BC$$
13. Write down number of flip flops are required to count 16 clock pulses.
14. List the types of DAC
15. Define Half adder and draw block diagram