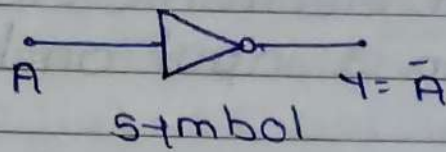


2] Logic Gate and Logic Families

Families.

- **Logic Gate**:- It is an electronic circuit having one or more than 1 input and only one output.
 - The relationship between input and output is based on certain logic
 - **Truth table**:- It is the table used to understand the operation of logic gate.
 - Truth table consist of all possible combination of inputs and corresponding steps of output of logic gate
 - **boolean Expression**:- The relation between input and output of gate can be expressed mathematically by using boolean Expression
 - **Types of logic Gate**:- (Classification)
 - Logic gate are classified into three types
 - A] Basic Gate
 - i] NOT Gate
 - ii] OR Gate
 - iii] AND Gate
 - B] universal Gate
 - i] NOR Gate
 - ii] NAND Gate
 - c] special purpose Gate.
 - i] Ex-OR gate
 - ii] Ex-NOR gate
- ∴ (Ex = Explosive)

a] 1] NOT gate or (Inverter):





• Truth table.

Input	output	$\bar{0} = 1$
A	$Y = \bar{A}$	$\bar{1} = 0$
0	1	
1	0	

2/8/23

2] AND gate

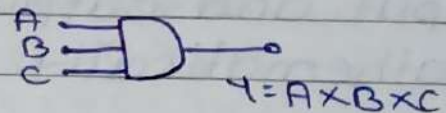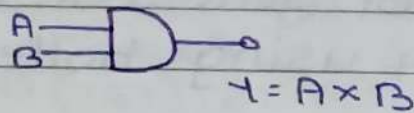

2-input AND-Gate
Symbol

3-input AND-Gate
Symbol


Truth table

Truth table.

input		output
A	B	$Y = A \times B$
0	0	0
0	1	0
1	0	0
1	1	1

Input			output
A	B	C	$Y = A \times B \times C$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

3] OR gate

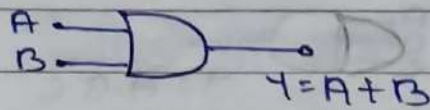

Truth table


Input		output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Truth table


input			output
A	B	C	$Y = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

6]

14] NOR gate

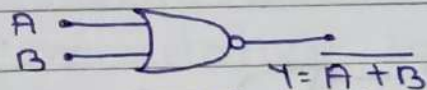



2-input NOR gate
Symbol

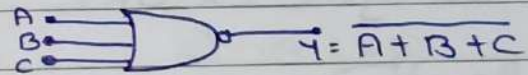

Input		output
A	B	$Y = A + B$
0	0	1
0	1	0
1	0	0
1	1	0

Input			output
A	B	C	$Y = A + B + C$
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0



2] NAND gate :-

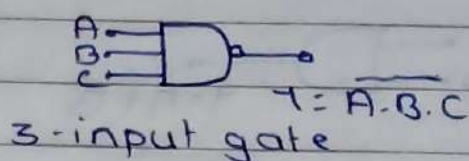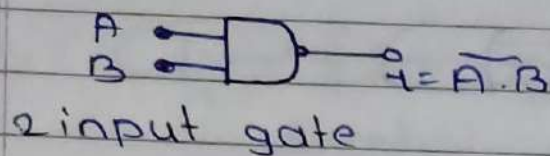

input		output	
A	B	$Y = \overline{A.B}$	
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

input			output	
A	B	C	$Y = \overline{A.B.C}$	
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0


c] i] Ex-OR gate (X-OR)

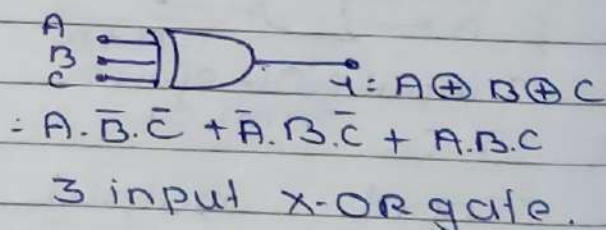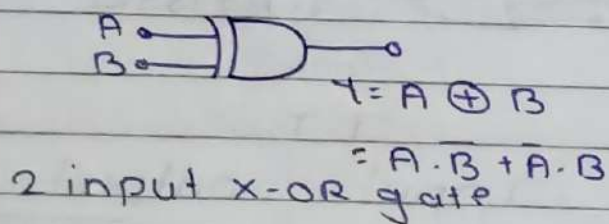

input		output
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

input			output
A	B	C	$Y = A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

ii] Ex-NOR gate (X-NOR)

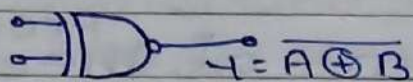

$$= A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

TT

Input		output	
A	B	$A \oplus B$	$Y = \overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

TT

input			output	
A	B	C	$A \oplus B \oplus C$	$Y = \overline{A \oplus B \oplus C}$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

* boolean laws :-

1] Commutative law

$$A \cdot B = B \cdot A$$

$$A + B = B + A$$

5] OR-Law

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \bar{A} = 1$$

2] Associated law

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$(A + B) + C = A + (B + C)$$

6] Inversion law

$$\bar{\bar{A}} = A$$

$$\bar{\bar{B}} = B$$

3] Distributive law

$$A(B + C) = AB + AC$$

ex: $\bar{0} = \bar{1} = 0$

4] AND Law

$$A \times 0 = 0$$

$$A \times 1 = A$$

$$A \times A = A$$

$$A \times \bar{A} = 0$$

3/8/23

* De-Morgan's Theorem:-

- 1] Theorem - I:- Complement of the ^{Product} theorem is equal to addition of complement

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

L.H.S					R.H.S	
A	B	\bar{A}	\bar{B}	$A \cdot B$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

$$\therefore \overline{A \cdot B} = \bar{A} + \bar{B}$$

- 2] Theorem - II :- Complement of sum is equal to product of complement

$$\overline{A + B} = \bar{A} \times \bar{B}$$

A	B	\bar{A}	\bar{B}	$A + B$	$\overline{A + B}$	$\bar{A} \times \bar{B}$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

- * Principle of Duality:- it states that in two value boolean Algebra the dual of an algebraic expression can be obtained by interchanging ~~or~~ OR and AND operator and by replacing 1 by 0 and 0 by 1

According to principle of duality the following conversion are possible in given boolean expression.

- 1) change each AND operation to OR operation
- 2) change each OR operation to AND operation
- 3] Complement any 1 OR 0 appear in the expression.

- duality theorem is useful in creating new expression from Given boolean Expression

1) $A + \bar{A} \cdot B = A$

→ L.H.S $A + A \cdot B$
 $A(1 + B)$

$= A \cdot 1 \quad \dots \{ 1 + B = 1$

$= A$

$= R.H.S$

2] $(A+B)(A+C) = A + BC$

→ L.H.S $(A+B)(A+C)$

$= A \cdot A + A \cdot C + B \cdot A + B \cdot C$

$= \boxed{A + A \cdot C} + B \cdot A + B \cdot C \quad \{ A \cdot A = A$

$= A + AB + BC \quad \dots \{ A + AC = A$

$= A + BC \quad \{ A + AB = A$

$= R.H.S$

3] $\bar{A} + AB = \bar{A} + B$

→ L.H.S $= \bar{A} + AB$

$= \boxed{\bar{A} \times 1} + AB$

$= \bar{A}(1+B) + AB \quad \{ 1+B=1$

$= \bar{A} + \bar{A}B + AB$

$= \bar{A} + B(\bar{A} + A)$

$= \bar{A} + B(1) \quad \dots \{ \bar{A} + A = 1$


$= \bar{A} + B$

$= R.H.S$



4/8/23

* Universal gate :- NAND gate and NOR gate are called universal gate because it is possible to implement any boolean expression by using only NAND gate and only NOR gate hence user can build any combination circuit by using only NAND gate or only NOR gate. hence it is not necessary for user to make stop of other gates than NAND gate or NOR gate


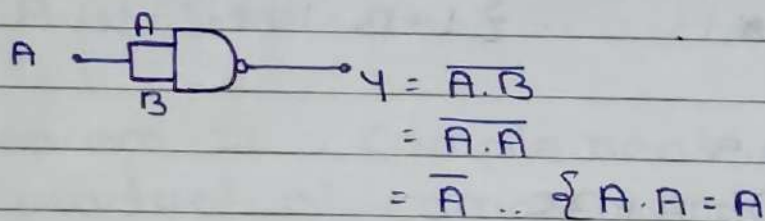
- NAND gate as universal gate:-
1) NOT gate using NAND gate



2] AND gate using NAND gate

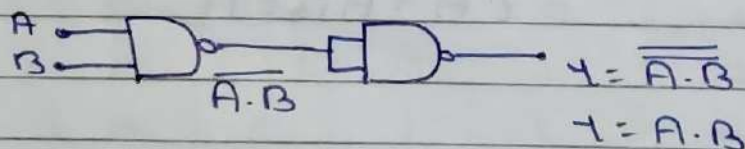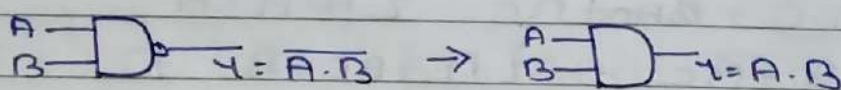


3] OR gate using NAND gate

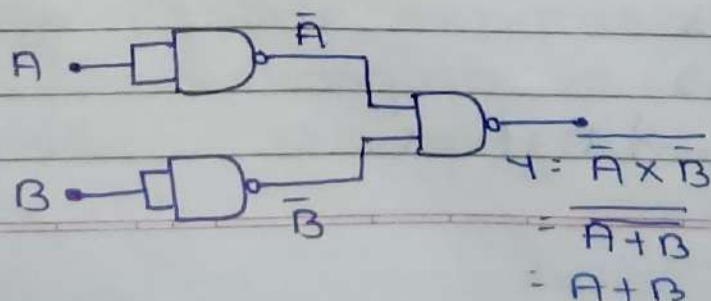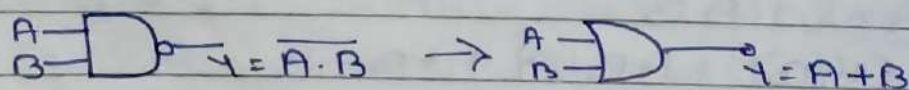

By De Morgan's theorem
 $\{ \overline{\overline{A+B}} = A+B \}$


4] NOR gate using NAND gate
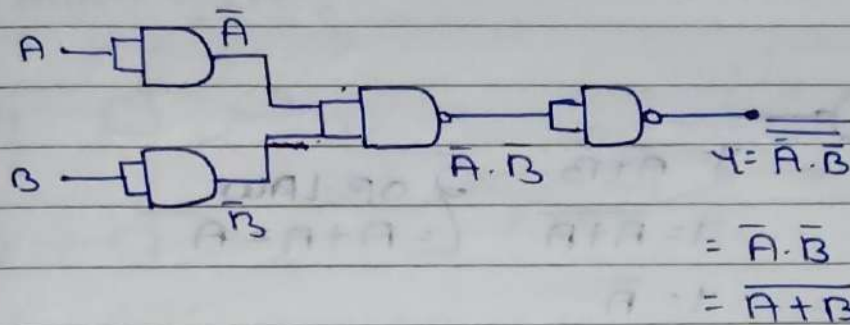
$$\begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = \overline{A \cdot B} \rightarrow \begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = \overline{A + B}$$




5] Ex-OR gate using NAND gate
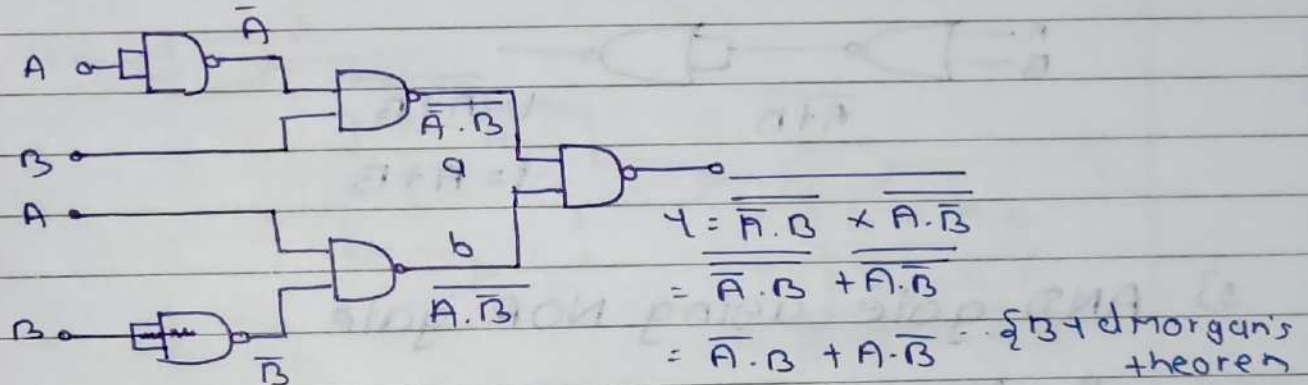
$$\begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = \overline{A \cdot B} \rightarrow \begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = A \oplus B = \overline{A}B + A\overline{B}$$




6] Ex-NOR gate using NAND gate
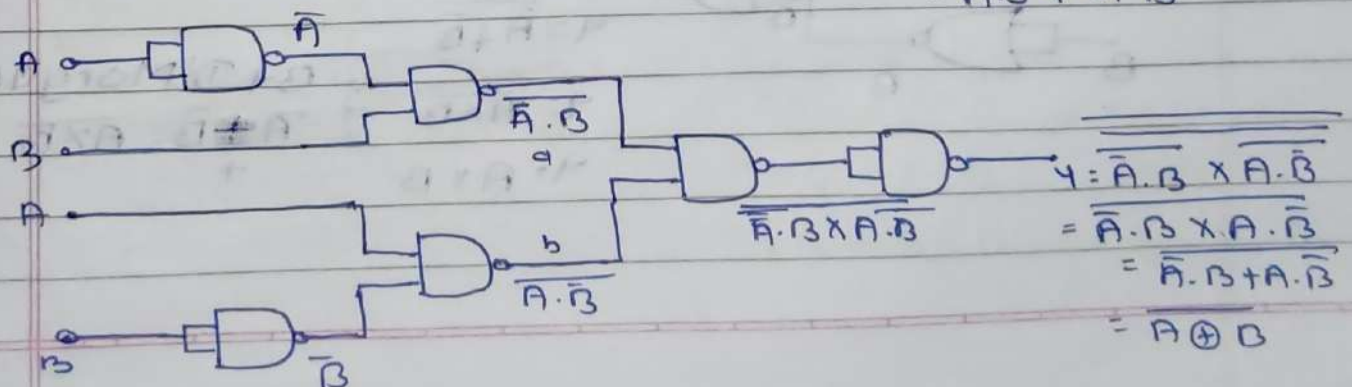
$$\begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = \overline{A \cdot B} \rightarrow \begin{matrix} A \\ B \end{matrix} \rightarrow \text{NAND} \rightarrow Y = \overline{A \oplus B} = \overline{\overline{A}B + A\overline{B}}$$




5/8/23

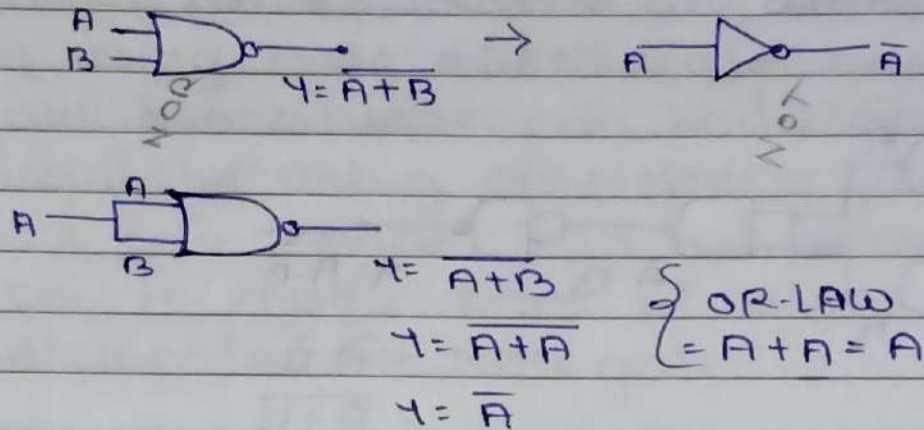
- * NOR gate as universal gate
 1) NOT gate using NOR gate.






- 2] OR gate using NOR gate

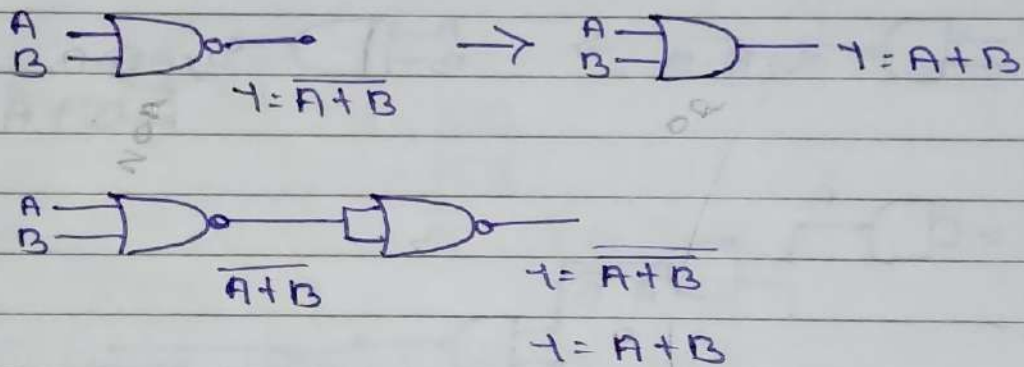



- 3] AND gate using NOR gate

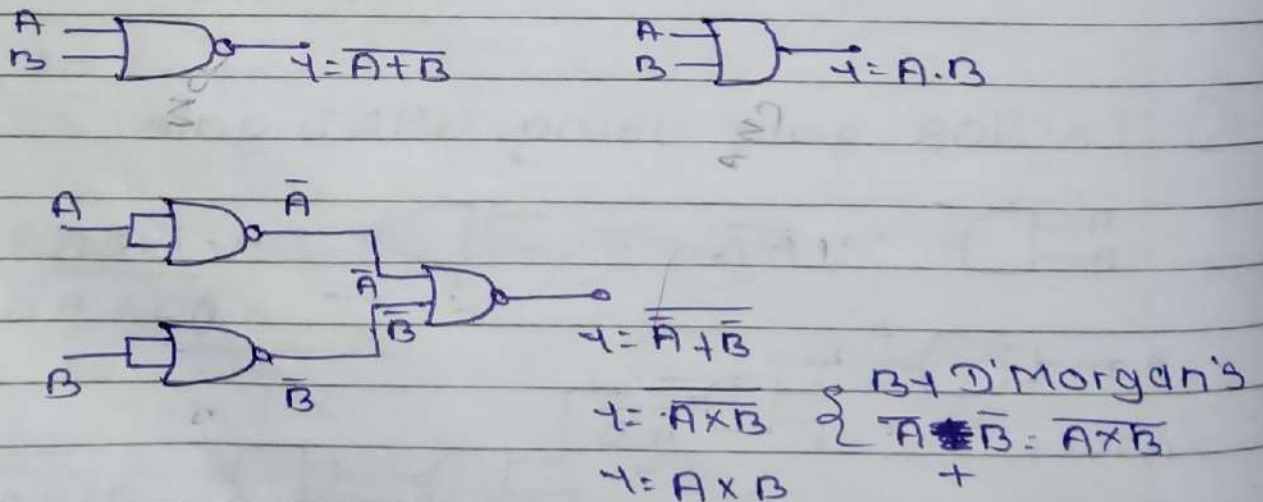


4] NAND using NOR gate

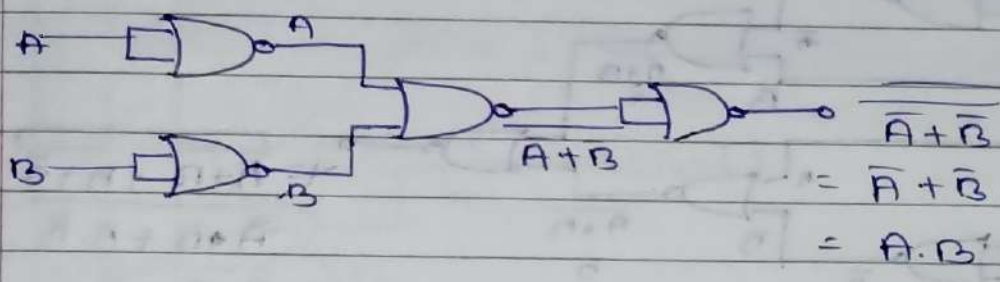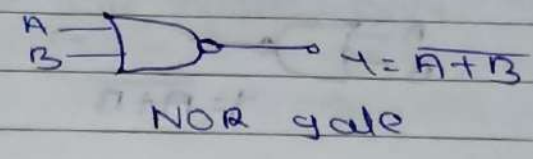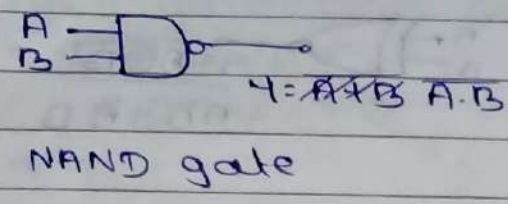


5] Ex-OR gate using NOR gate

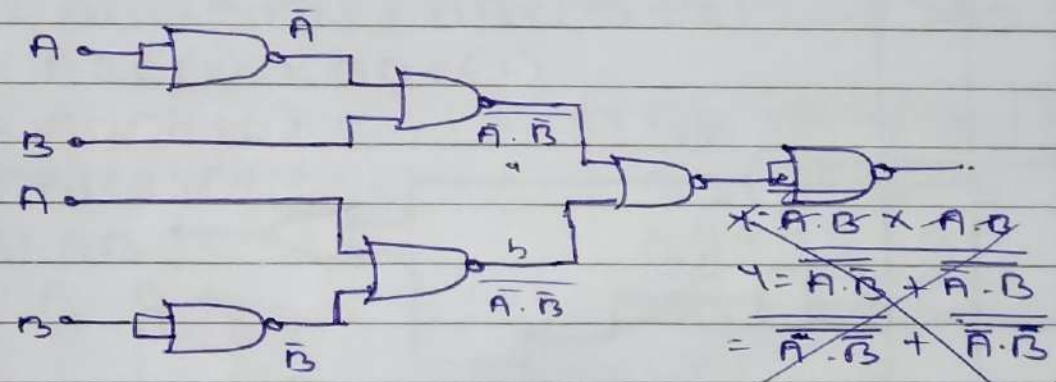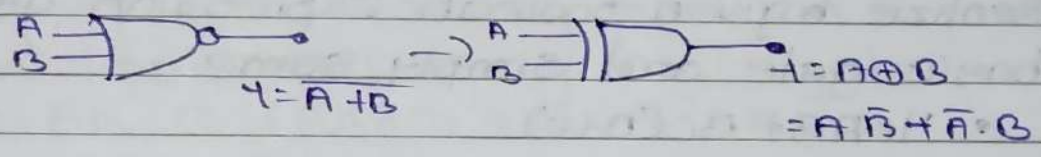

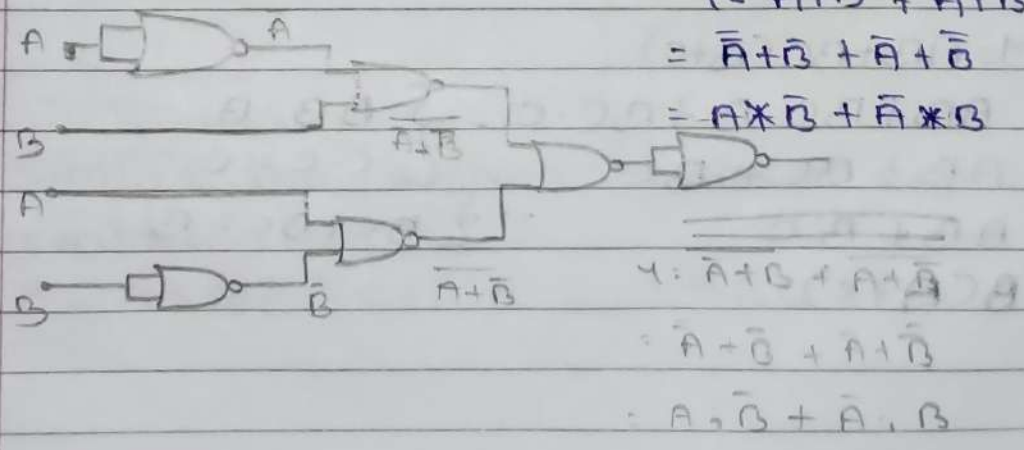~~$$\begin{aligned}
 Y &= \overline{A \cdot B + A \cdot B} \\
 &= \overline{A \cdot B} + \overline{A \cdot B} \\
 &= \overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{B} \\
 &= \overline{A} \cdot \overline{B} + \overline{A} \cdot \overline{B} \quad \text{By De Morgan's theorem}
 \end{aligned}$$~~



Ex-NOR gate using NOR gate.

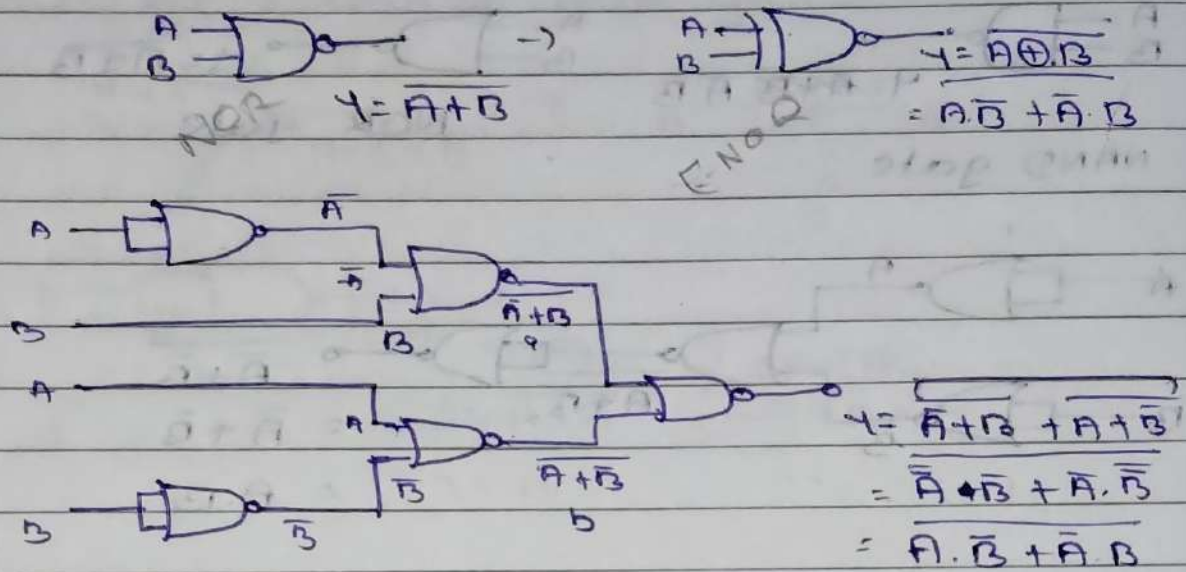


6/8/23

★ ★
S22
4 marks

Realize the given boolean Expression using basic gate and simplify same

• $Y = AB + BC(B+C)$

A B C

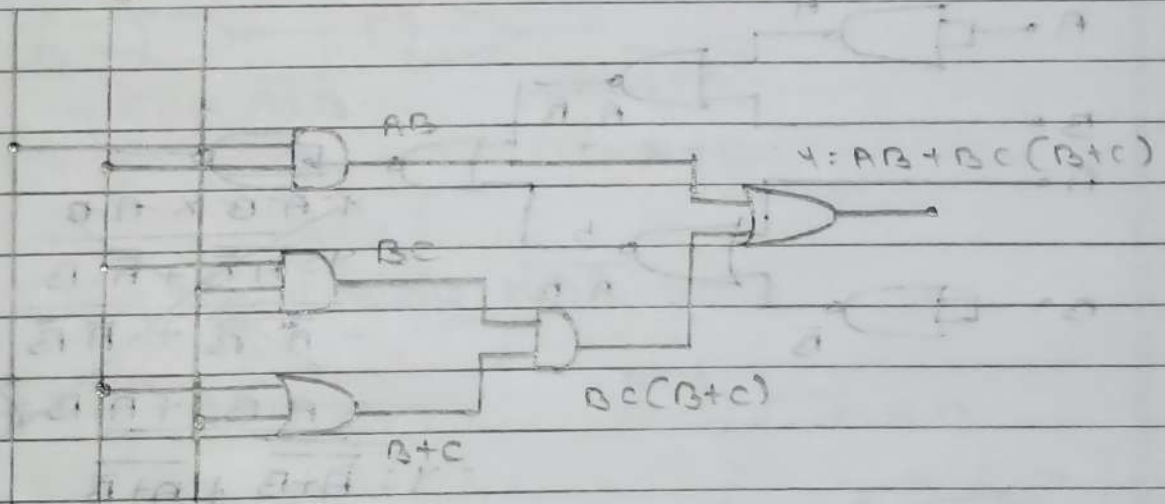

$Y = AB + BC(B+C)$

$= AB + BC \cdot B + BC \cdot C$ $\left\{ \begin{array}{l} BB = B \\ CC = C \end{array} \right.$

$= AB + BC + BC$

$= AB + BC$

$= B(A+C)$


$\therefore B + B = B$

2] sketch the ^{given} boolean expression using one AND gate and one OR gate only.

$$Y = AB + AC$$

$$= A(B+C)$$

A B C

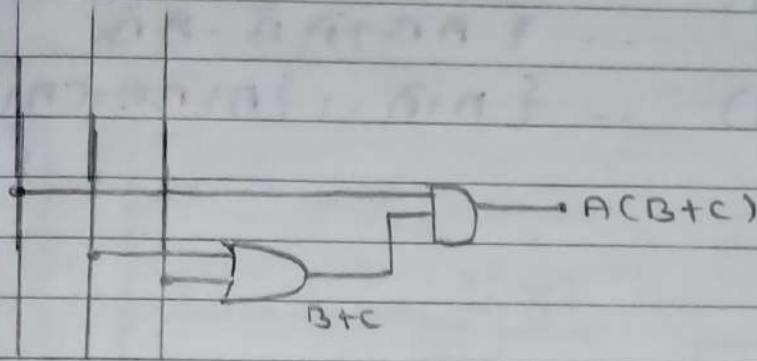

3] Simplify the following boolean Expression and implement using logic gate.

$$Y = AB\bar{C}\bar{D} + AB\bar{C}D + AB\bar{C}\bar{D} + AB\bar{C}D$$

$$= AB\bar{C}[\bar{D} + D] + AB\bar{C}[\bar{D} + D] \quad \therefore \{\bar{D} + D = 1\}$$


$$= AB\bar{C}(1) + AB\bar{C}(1)$$

$$= AB\bar{C}(\bar{C} + C)$$

$$= AB \times 1$$

$$Y = AB$$

A B

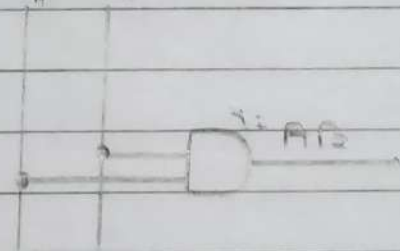


$$Y = AB + BC(B+C)$$

$$AB + BC \cdot B + BC \cdot C$$

$$AB + BC + BC$$

$$AB + BC$$

$$AB + BC(B+C)$$

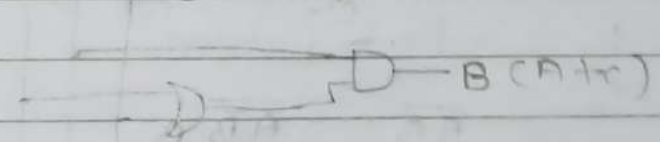

4] Simplify the given boolean expression and realize it.

$$Y = A + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC + \bar{A}\bar{B}$$

$$Y = A + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC + \bar{A}\bar{B}$$

$$A + ABC + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}$$

$$= A(1+BC) + \bar{A}\bar{B}(C+\bar{C}) + \bar{A}\bar{B}$$

$$= A(1) + \bar{A}\bar{B}(1) + \bar{A}\bar{B} \quad \left\{ \begin{array}{l} 1+BC=1 \\ C+\bar{C}=1 \end{array} \right.$$

$$= A + \bar{A}\bar{B} + \bar{A}\bar{B}$$

$$= A + \bar{A}\bar{B}$$


$$\dots \bar{A}B + \bar{A}\bar{B} = \bar{A}$$

$$(A+\bar{A}) \cdot (A+\bar{B}) \dots \{ A+\bar{A}=1 \} \{ A+BC = (A+B)(A+C) \}$$



$$= 1(A+\bar{B})$$

$$Y = A + \bar{B}$$

A B

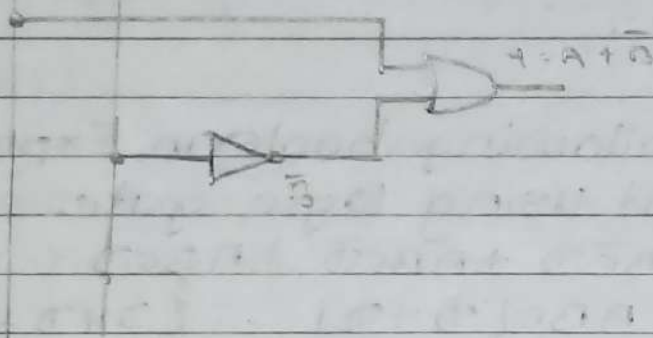

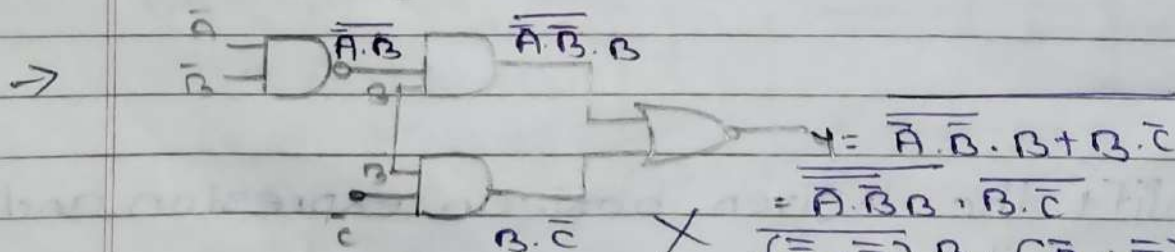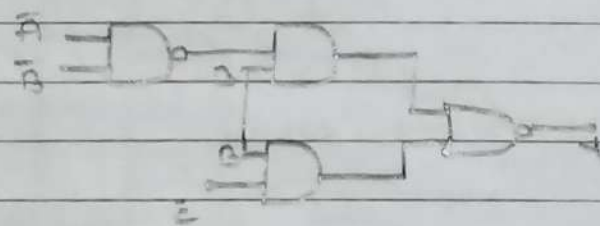- For given Figure derived boolean expression of Y



$$Y = \bar{A}\bar{B}.B + B.C$$

$$= \bar{A}\bar{B}B.B.C$$


$$= (\bar{A}+\bar{B})B.(C\bar{B}+\bar{C}). \{ \bar{A}\bar{B} + \bar{A}B \}$$

$$Y =$$

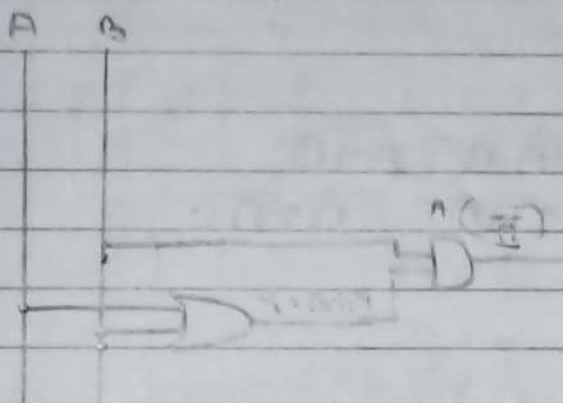Q.11 reduce the following boolean expression

$$Y = AB + \bar{A}B + A\bar{B} + \bar{A}\bar{B}$$

$$\begin{aligned} Y &= AB + \bar{A}B + A\bar{B} + \bar{A}\bar{B} \quad \{ \bar{A}B = B\bar{A} \} \\ &= B(A + \bar{A}) + A\bar{B} + \bar{A}\bar{B} \quad \{ A + \bar{A} = 1 \} \\ &= B(1) + A\bar{B} + \bar{A}\bar{B} \\ &= B + \bar{B}(A + \bar{A}) \end{aligned}$$



Simplify given boolean expression and realize it using logic gate.

$$ABC + \bar{A}\bar{B}C + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C}$$


$$\rightarrow ABC + AB\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$ABC + AB\bar{C} + \bar{A}\bar{B} [C + \bar{C}] \quad \{ ABC + AB\bar{C} = AB(C + \bar{C}) \}$$

$$AB[C + \bar{C}] + \bar{A}\bar{B}(C) \quad \{ C + \bar{C} = 1 \}$$

$$AB(1) + \bar{A}\bar{B}$$

$$AB + \bar{A}\bar{B}$$

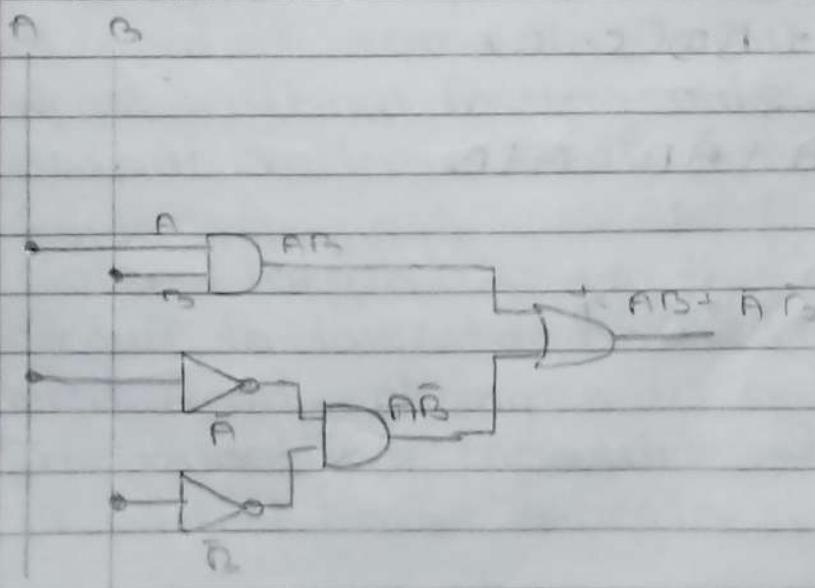

$$Y = \bar{A}\bar{B}C + B\bar{C} + \bar{A}BC + ABC$$

$$= \cancel{ABC} + \cancel{B\bar{C}} + \cancel{\bar{A}BC} + \cancel{\bar{A}\bar{B}C}$$

$$= B\bar{C}$$

$$= \bar{A}\bar{B}C + B\bar{C} + \bar{A}BC + ABC$$

$$= \bar{A}\bar{B}C + B\bar{C} + BC(\bar{A} + A)$$

$$= \bar{A}\bar{B}C + B\bar{C} + BC$$


$$= \bar{A}\bar{B}C + BC(\bar{C} + C)$$

$$= \bar{A}\bar{B}C + BC$$


$$= B + \bar{A}C$$

$$\left\{ \begin{array}{l} A + \bar{A}B = A + B \\ B + \bar{B}AC = B + \bar{A}C \end{array} \right.$$


A B C

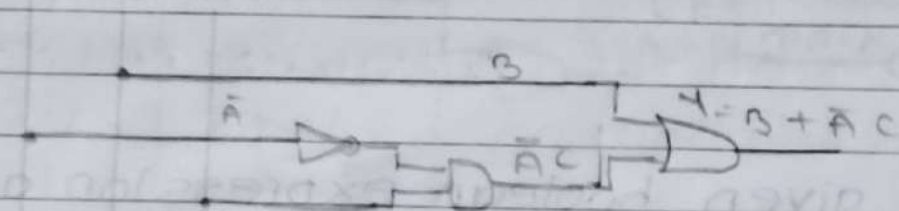

$$\begin{aligned} Y &= B\bar{C}\bar{D} + \bar{A}B\bar{D} + AB\bar{D} + B\bar{C}D + \bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C}D \\ &\quad + B\bar{C}\bar{D} + B\bar{C}D + \bar{A}B\bar{D} + AB\bar{D} + \bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C}D \\ &= B\bar{D}(\bar{C} + C) + B\bar{D}(\bar{A} + A) + \bar{B}C\bar{D} + \bar{B}C\bar{D}(\bar{A} + A) \\ &= B\bar{D} + B\bar{D} + B\bar{C}\bar{D} + \bar{B}\bar{C}\bar{D} \\ &= B(\bar{D} + D) + \bar{B}\bar{D}(C + \bar{C}) \\ &= B + \bar{B}\bar{D} \\ &= B + \bar{D} \quad \because A + \bar{A}B = A + B \end{aligned}$$

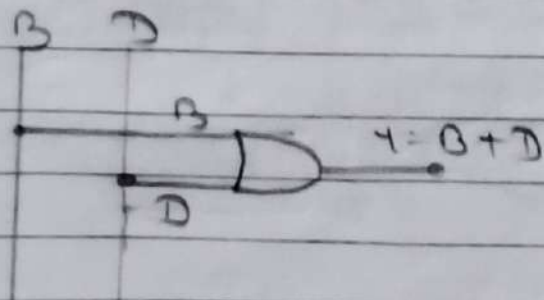
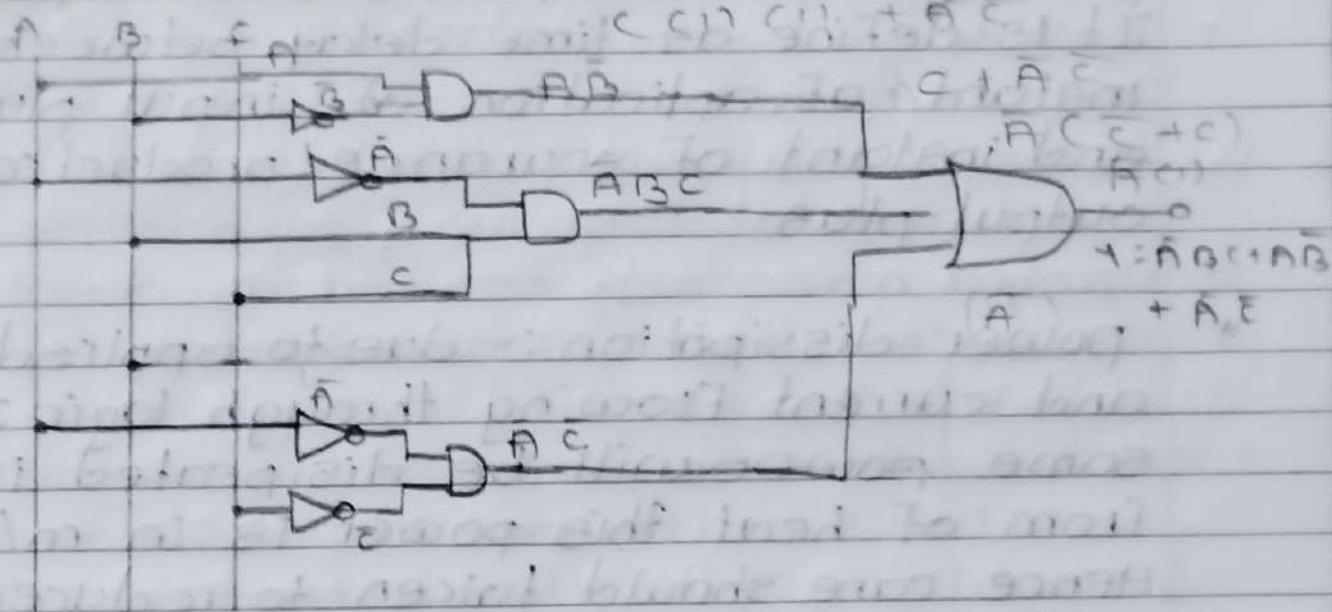
$$Y = \bar{A}BC + A\bar{B} + \bar{A}\bar{C} \quad \text{or} \quad (\bar{A}+A)(\bar{B}+B) + \bar{A}\bar{C}$$



[IC] = Integrated circuit

8/8/23

logic family's

- Various digital ICs available in market are on different types this types are known as family's
- characteristics of digital IC
- * 1] fan-in: It is define as the no of inputs a get as
Ex: three input get has fan in equal to 2_{max}
- * 2] fan-out: It is define as the no of input of same IC family that get can drive without falling outside the specified output voltage limit.
- (noise immunity)
- * Noise Margin: It is the ability of logic circuit to tolerate noise without causing any changes in output.
- The quantitative measure of noise margin is called noise margin

* propagation delay (Speed of operation)
 - It is defined as time delay between instant of application of input plus and instant of occurrence/production of output plus

* power dissipation :- due to applied voltage and current flowing through logic IC some power will be dissipated in the form of heat this power is in m/W Hence care should be taken to reduce power dissipation taking place in IC to protect IC.

* Figure of merit :- It is the product of propagation delay and power dissipation is called Figure of merit.

$$\text{Figure of merit} = \frac{\text{propagation delay}}{\text{power dissipation}}$$

Difference between TTL and CMOS logic family

Parameter	TTL	CMOS
1] Basic gate	NAND	NOR/NAND
2] propagation delay	10 nanos/nls	70 nls
3] fan out	10	50
4] power dissipation per gate	10 mW	0.1 mW
5] Speed power product (Figure of merit)	100 pJ (pico Joule)	0.7 pJ

6]	Noise immunity	0.2V	5V
----	----------------	------	----

Questions.

W-22.1] Sketch the ^{given} boolean expression using one AND gate and one OR gate only

$$Y = AB + AC + A(B+C)$$

4marks 2] Realize the following operation using ~~AND~~ only NOR gate ~~AND~~ OR, NOT

3] Draw symbol truth table and logical output equation of OR and X-OR gate.

4] Write difference betⁿ TTL and CMOS logic families on the basis of Fan out, propagation delay, power dissipation and Figure of merit.

5] State and prove D. Morgan's theorem.

6] Draw basic gates AND, OR, NOT using NAND gate only

7] realize the given boolean expression using basic gate and simplify the same.

$$Y = AB + BC(B+C)$$

8] Compare TTL and CMOS with following points

Fan out, basic gate, propagation delay and power dissipation.

W-19.9] Draw symbol truth table and logic eqⁿ of ex-OR gate


10] State D-Morgan's theorem.

11] Simplify the following boolean expression and implement using logic gate

$$Y = ABC\bar{D} + AB\bar{C}D + ABC\bar{D} + ABCD$$

$$= AB\bar{C}(\bar{D} + D) + ABC(\bar{D} + D)$$
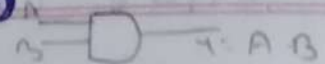
$$= AB\bar{C}(1) + ABC(1) = AB\bar{C} + ABC = AB$$



- 12] realize the following expression using only NAND gate, OR, AND, NOT.
- 13] compare TTL and CMOS logic Family on the basis of following point.
basic gate, pd, fan out, power d, Noise immunity, and speed power product.
- 14] Define Fan in and Fan out of a gate.
- 15] Draw logical symbol and x-OR and x-NOR gate.
- 16] Simplify the following and realize it.
 $Y = A + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}\bar{B}$
- 17] Explain the following characteristic with respect to:
1] Noise margin, 2] Pd 3] SOF operation 4] Figure of merit.
- 18] state and Prove D. Morgan's theorem.
- 19] Design basic logic gate using NAND and NOR gate.
- 20] Draw the symbol of AND gate and OR gate.
- 21] Draw the symbol, truth table and logic expression of any one universal logic gate. write reason why it is called universal gate.
- 22] compare TTL and CMOS logic family's on the basis of Pd, power d, Fanout, and basic gate.
- 23] realize the basic logic gate by using NOR gate only.
- 24] state and prove D. Morgan's theorem.

5. Q. 1] Compare TTL and CMOS on the basis of
 P.d. Power d. Fan out & basic gate.
- 2] realize the basic gate using only NAND
 gates. 3] Draw symbols truth table and
 3] logic expression on two input universal
 gate.
- 3] Reduce the Follow boolean expression

$$Y = AB + \bar{A}B + A\bar{B} + \bar{A}\bar{B}$$